

170050068 - Assignment : Sequence Detection

X = "101010101111001001010011"

Input :

Seq : 1072 bit std_logic_vector (1000 + 24 +24 + 24)

Clk : 1 bit std_logic

Output :

Det : 1 bit std_logic (Updates for every clock cycle based on input bit).

States :

A,B,C,D,E,F,G,H,I,J,K,L,M,N,O,P,Q,R,S,T,U,V,W,X

5 bits are used to represent the states.

abcdef is a 5 bit vector

Present state	a	b	c	d	e	Input(f)	Output(Y)	Next state
A	0	0	0	0	0	0	0	A
A	0	0	0	0	0	1	0	B
B	0	0	0	0	1	0	0	C
B	0	0	0	0	1	1	0	B
C	0	0	0	1	0	0	0	A
C	0	0	0	1	0	1	0	D
D	0	0	0	1	1	0	0	E
D	0	0	0	1	1	1	0	B
E	0	0	1	0	0	0	0	A
E	0	0	1	0	0	1	0	F
F	0	0	1	0	1	0	0	G
F	0	0	1	0	1	1	0	B
G	0	0	1	1	0	0	0	A
G	0	0	1	1	0	1	0	H
H	0	0	1	1	1	0	0	I
H	0	0	1	1	1	1	0	B
I	0	1	0	0	0	0	0	A
I	0	1	0	0	0	1	0	J
J	0	1	0	0	1	0	0	I
J	0	1	0	0	1	1	0	K
K	0	1	0	1	0	0	0	C
K	0	1	0	1	0	1	0	L
L	0	1	0	1	1	0	0	C
L	0	1	0	1	1	1	0	M
M	0	1	1	0	0	0	0	N

M	0	1	1	0	0	1	0	B
N	0	1	1	0	1	0	0	O
N	0	1	1	0	1	1	0	D
O	0	1	1	1	0	0	0	A
O	0	1	1	1	0	1	0	P
P	0	1	1	1	1	0	0	Q
P	0	1	1	1	1	1	0	B
Q	1	0	0	0	0	0	0	R
Q	1	0	0	0	0	1	0	D
R	1	0	0	0	1	0	0	A
R	1	0	0	0	1	1	0	S
S	1	0	0	1	0	0	0	T
S	1	0	0	1	0	1	0	B
T	1	0	0	1	1	0	0	A
T	1	0	0	1	1	1	0	U
U	1	0	1	0	0	0	0	V
U	1	0	1	0	0	1	0	B
V	1	0	1	0	1	0	0	W
V	1	0	1	0	1	1	0	F
W	1	0	1	1	0	0	0	A
W	1	0	1	1	0	1	0	X
X	1	0	1	1	1	0	0	C
X	1	0	1	1	1	1	0	A

State Equations:

$$Y(t+1) = acdef$$

$$a(t+1) = ac'e'f + ac'ef + ad'ef + acd'f + bcdef + acde'f$$

$$b(t+1) = bc'f + bc'd'e + bde'f + bcd'f + a'b'cdef$$

$$c(t+1) = cd'ef + cde'f + bcd'f + acd'f + acd'e + a'b'ce'f + bc'def + ac'def + a'b'c'def$$

$$d(t+1) = a'de'f + cd'ef + cde'f + bd'ef + bc'df + ac'd'f + ad'ef + acef + a'b'd'ef + ac'de'f$$

$$e(t+1) = e'f + a'b'f + a'cf + ac'e' + ad'e' + bcd'e'$$

State Diagram:

